

(DC1-3) Determination of Unknown Resistance, Meter Bridge

Aim of experiment

Determination of an unknown resistance using a Meter Bridge

Tools

Meter Bridge – D.C power supply – set of standard resistances – unknown resistance – galvanometer or sensitive voltmeter.

Theory of experiment

ABCD, *figure 1*, is a diagrammatic form of the *Wheatstone bridge*. At the point of balance, i.e. when the galvanometer shows no deflection, we find that

$$V_{AB} = V_{AD}, \quad I_1 R_1 = I_2 R_3 \quad (1)$$

$$V_{BC} = V_{DC}, \quad I_1 R_2 = I_2 R_4 \quad (2)$$

From (1) and (2)

$$R_1 / R_2 = R_3 / R_4 \quad (3)$$

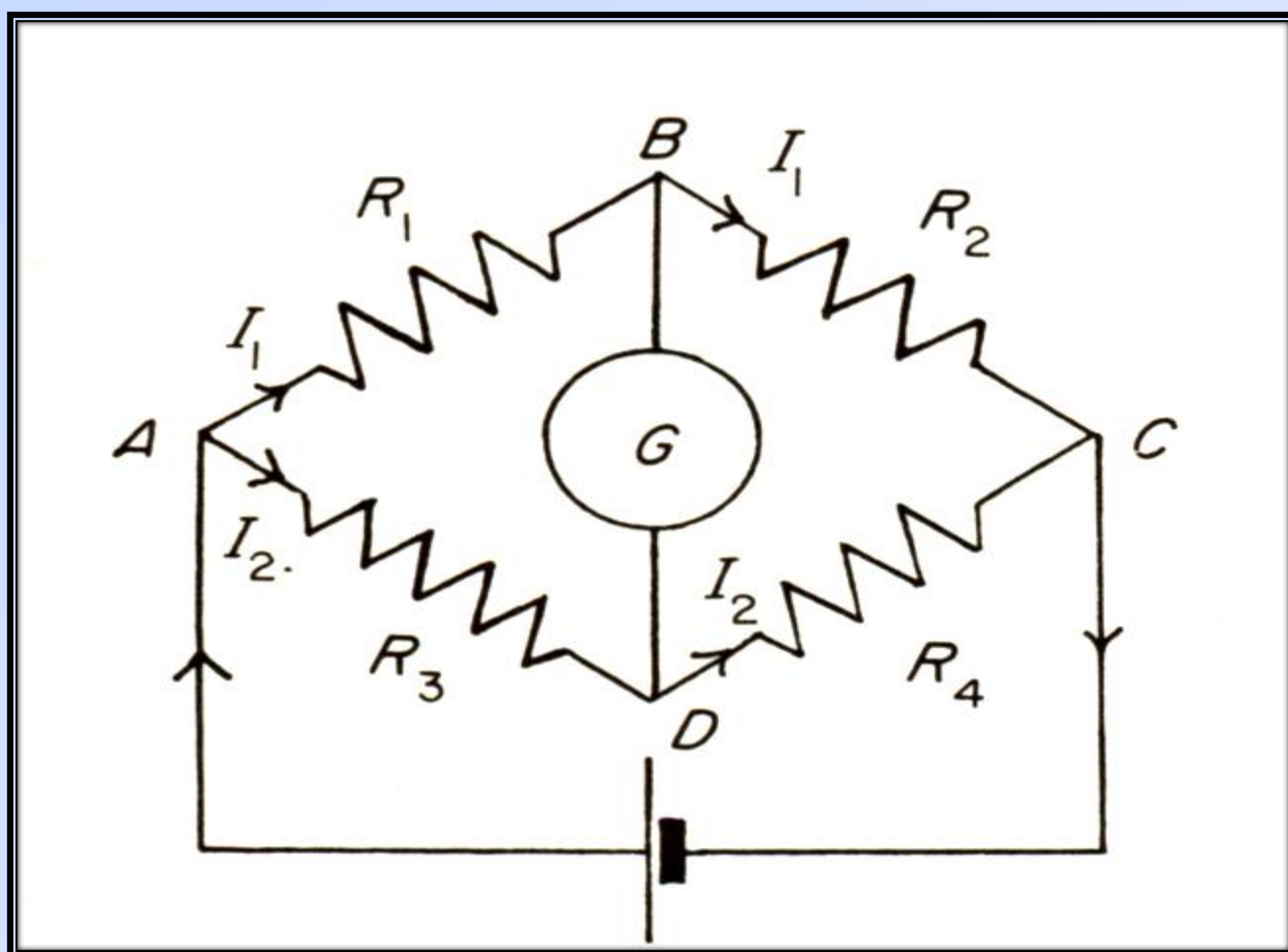


Figure 1 Wheatstone bridge

The meter bridge of *figure 2* is a special case of Wheatstone bridge, *figure 1*. If the wire of meter bridge has a uniform cross section, then its resistance is proportional to its length

Equation (3) then yields

$$R_1 / R_2 = l_1 / l_2 \quad (4)$$

So if R_1 is known and R_2 is unknown and at the point of balance, l_1 and l_2 are measured, then one can determine the unknown resistance, R_2 .

The resistance R_2 can be a result of series or parallel connection of known resistances, so one can verify the series and parallel resistances connection laws.

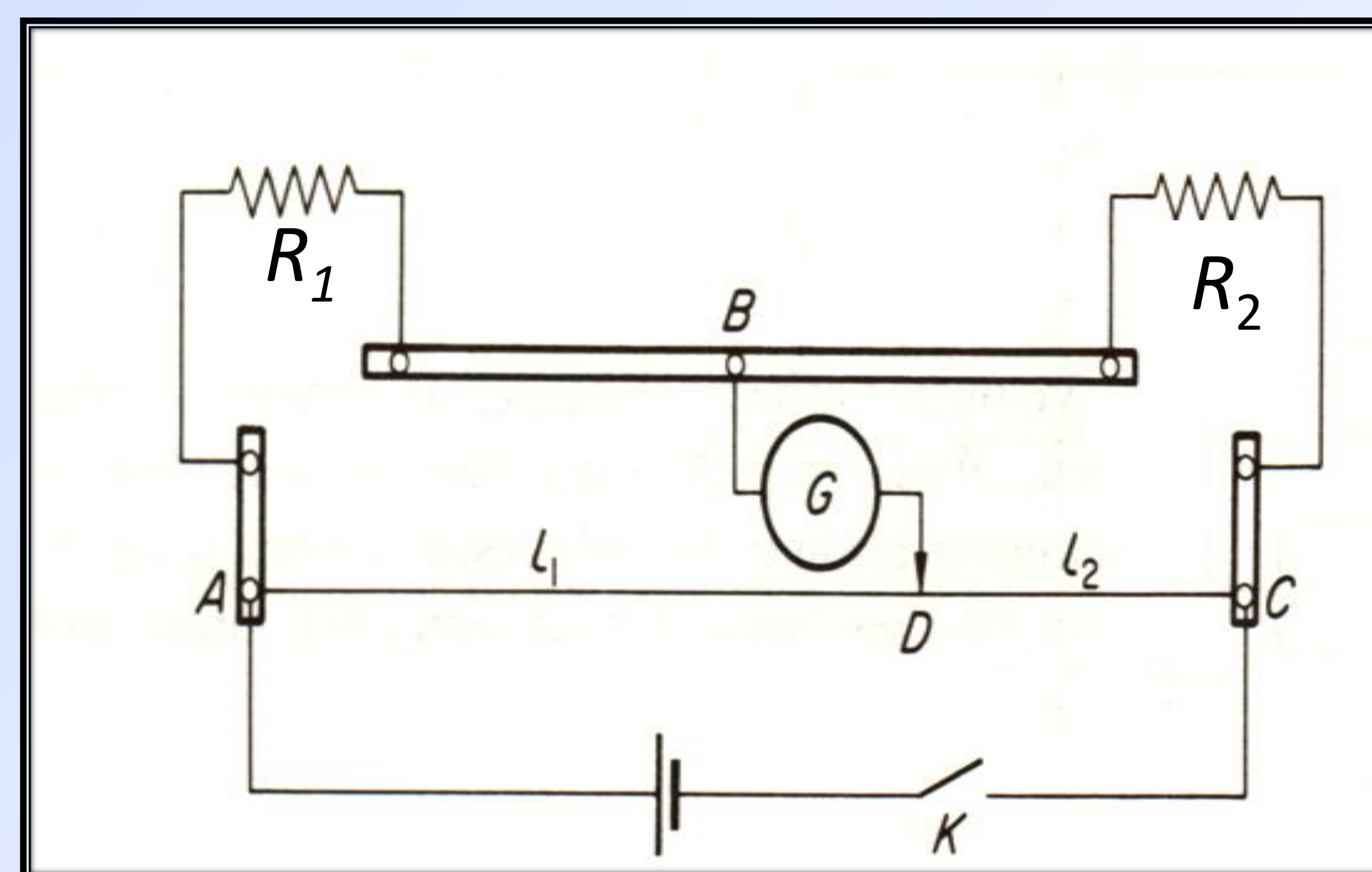


Figure 2 Meter bridge

Procedures

- 1- Switch on the circuit power
- 2- Connect up the bridge as shown in *figure (1)*
- 3- Check all connections, and adjust the power supply on ≈ 1 Volt.
- 4- Insert the first unknown resistance R_{21}

5- Move the slider along the wire until a point of balance is obtained.

5- Measure l_1 and l_2

6- Determine the value of unknown resistance R_{21} from equation (4).

7- Repeat the previous steps to determine the resistances R_{22} .

8- Repeat the previous steps to determine the equivalent of R_{21} and R_{22} resistances connected in series and parallel in place of resistance R_2 .

Results

1- First resistance R_{21}

$$R_3 = \quad \Omega$$

At balance

$$l_1 = \quad \text{cm} \quad \text{and} \quad l_2 = \quad \text{cm}$$

$$R_{21} = \quad \Omega$$

2- Second resistance R_{22}

$$R_3 = \quad \Omega$$

At balance

$$l_1 = \quad \text{cm} \quad \text{and} \quad l_2 = \quad \text{cm}$$

$$R_{22} = \quad \Omega$$

3- For series connection

$$R_3 = \quad \Omega$$

At balance $R_{2s} = \quad \Omega$

4- For parallel connection

$$R_3 = \quad \Omega$$

At balance

$$l_1 = \quad \text{cm} \quad \text{and} \quad l_2 = \quad \text{cm}$$

$$R_{2p} = \quad \Omega$$

5- Comment on the results