

(DC1-1) Measurement of Ohmic Resistances Using Ammeter and Voltmeter

Aim of experiment

- 1. Verification of Ohm's law
- 2. Verification of the law of series and parallel resistances connection.

Tools

Voltmeter-Ammeter-Power Supply - Resistors R_1 and R_2 .

Theory of experiment

OHM'S law states that when two points are taken on linear conductor, the ratio of the difference of potential, V , between those points to the current, I , flowing through the conductor is a constant. This constant ratio is termed the resistance, R , of the conductor. The reciprocal of R is the conductance.

A resistor is a piece of apparatus used on account of its possessing resistance. The most direct method of measuring resistance is to measure the potential difference, and the current. If a voltmeter measures the difference of potential in volts and the strength of the current in amperes, is measured by an ammeter, the resistance is in ohms.

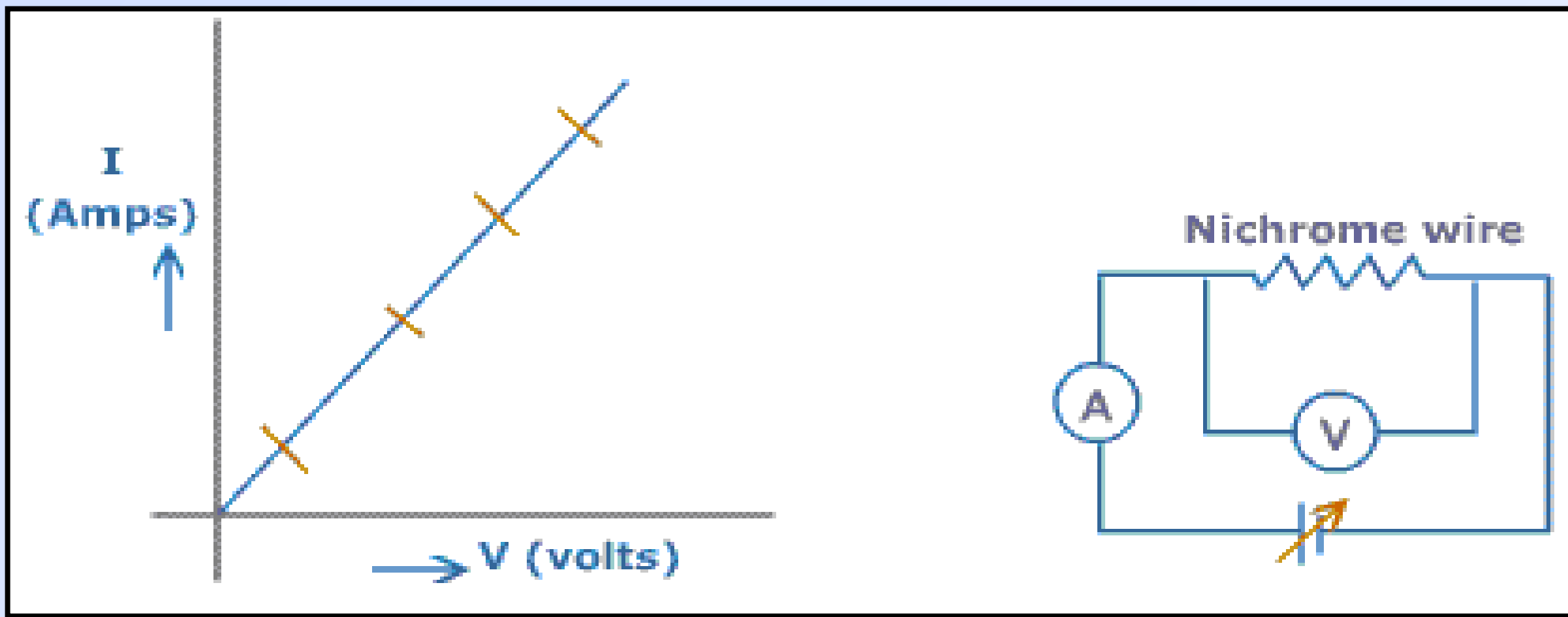


Figure 1. The I-V characteristic of an Ohmic resistance and the circuit diagram

Note carefully that the ammeter is con-nected in series with the resistance to be measured, while the voltmeter is connected across the ends of the resistance, so that, with a moving-coil instrument, the coil of the voltmeter is in parallel with the resistance.

The terminals marked + on the ammeter and the voltmeter must be connected to the + pole of the battery, or the power supply. In this method the resistance of the conductor is measured while a current is flowing through it. The method is therefore applicable in cases where other methods fail; for instance, we can measure in this way the resistance of an incandescent electric lamp while it is glowing. This is a rough method only, though very convenient in many cases. It depends on the observed deflections of the ammeter and voltmeter, and is thus not as accurate as a null method of measuring resistance. If the ammeter and voltmeter have not been calibrated, the result may be erroneous owing to errors of graduation.

Procedures

Experiment 1: Measurement of a resistance using ammeter and voltmeter_

- 1. Connect the circuit as shown in *figure 1*.

- 2. Using the rheostat, built in the power supply, adjust the voltage across the resistance, R_1 , to be 0.5 V and take the ammeter reading.
- 3. Increase the voltage at steps of 0.5V and notice the ammeter reading I.
- 4. Repeat step 3 at least three times and tabulate your results.
- 5. Plot the relation between V and I_{av} and determine the slope from which calculate the resistance R_1 .
- 6. Repeat the above steps for resistance R_2 .

Results

R1					R2				
V (V)	I ₁ (A)	I ₂ (A)	I ₃ (A)	I _{av} (A)	V (V)	I ₁ (A)	I ₂ (A)	I ₃ (A)	I _{av} (A)

(DC1-1) Measurement of Ohmic Resistances Using Ammeter and Voltmeter

Experiment 2: Verification of the law of the parallel and series resistance connections for R_1 and R_2 .

- 1- Repeat the above steps for R_1 and R_2 are connected in series and measure R_s .
- 2- Repeat the above steps for R_1 and R_2 are connected in parallel and measure R_p .
- 3- Verify the series and parallel connection laws.

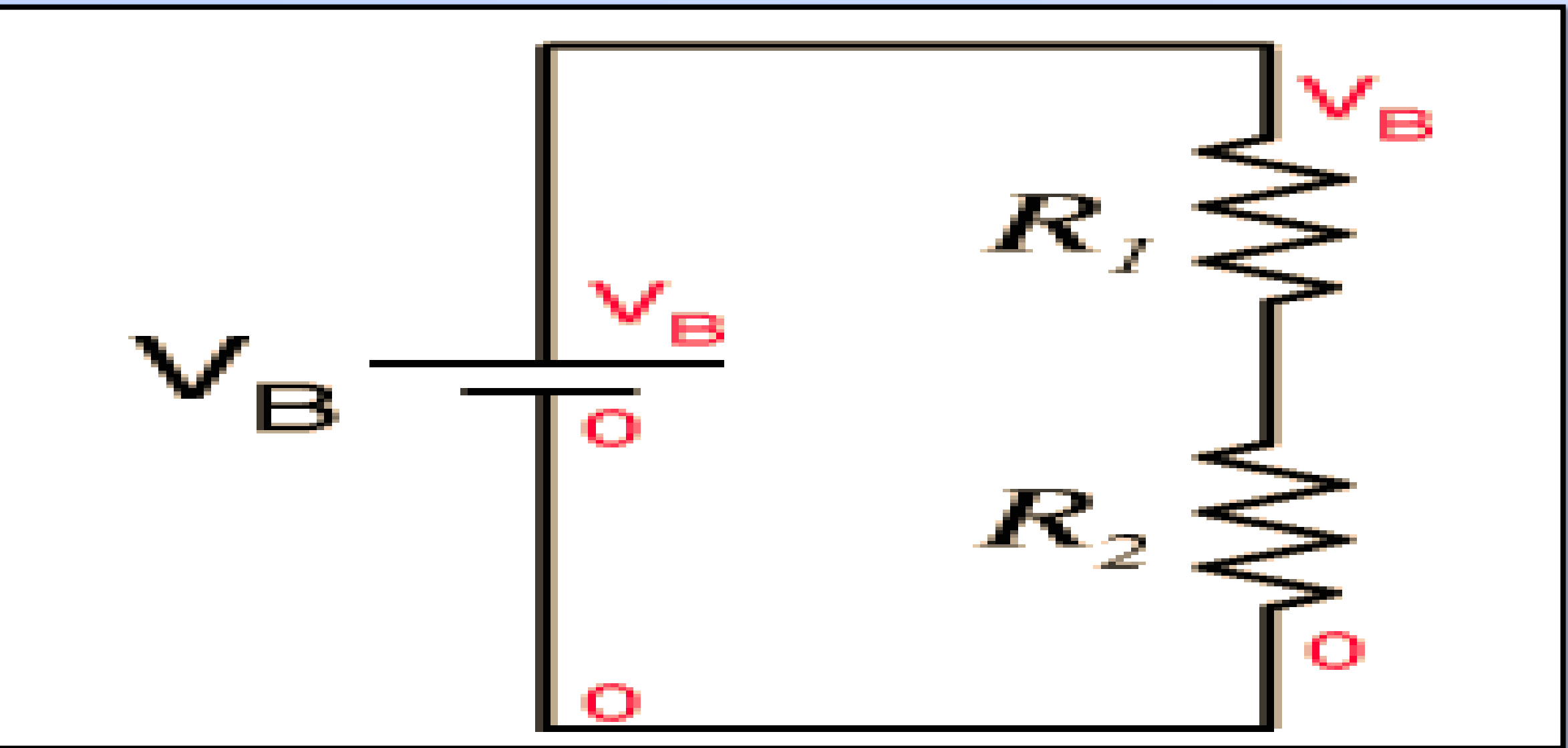


Figure 3. A circuit of series connection

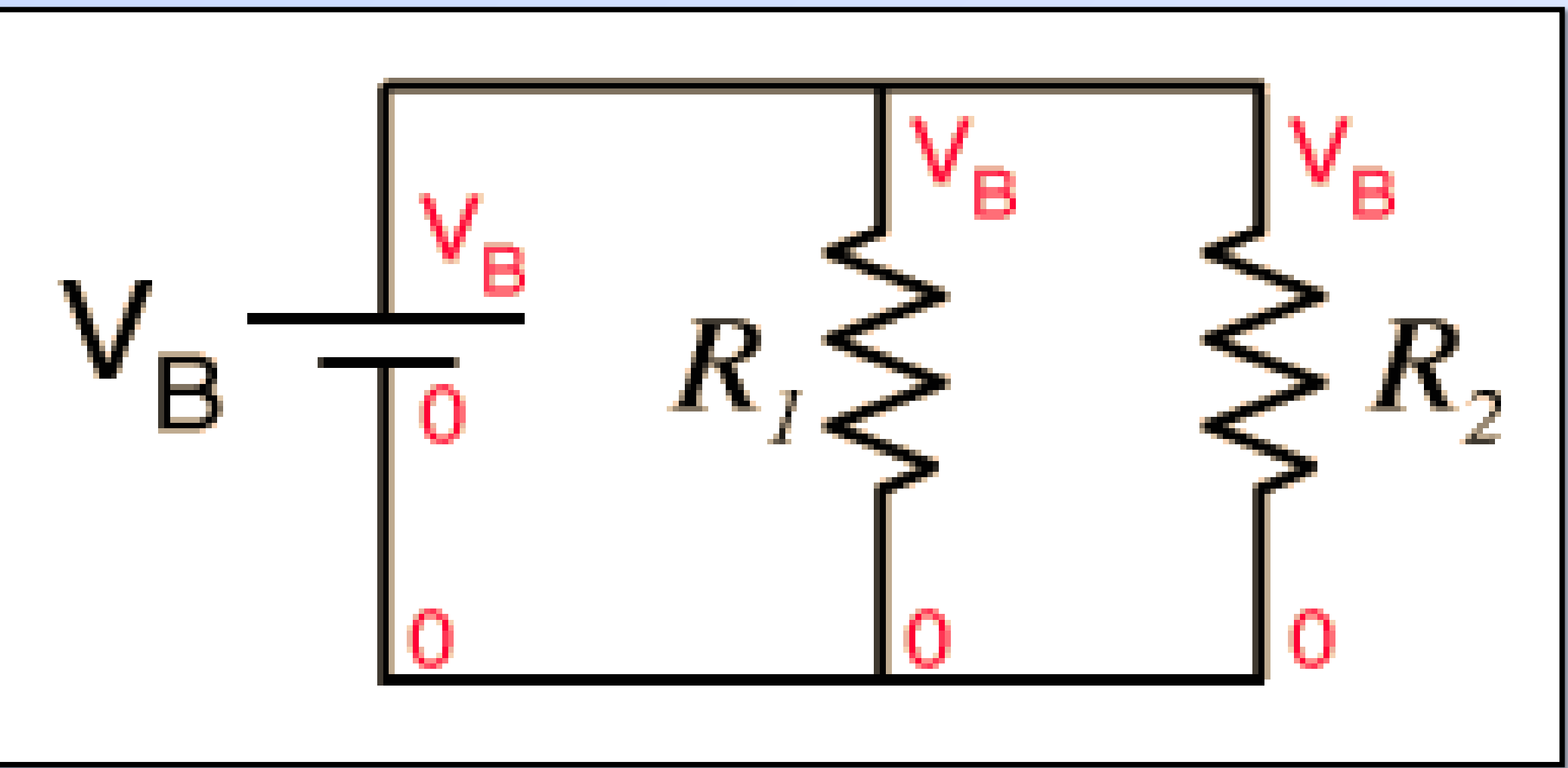


Figure 4. A circuit of parallel connection

Procedures

- 1- Repeat the above steps for R_1 and R_2 are connected in series and measure I and V and calculate R_s .
- 2- Repeat the above steps for R_1 and R_2 are connected in parallel and measure I and V and calculate R_p .
- 3- Verify the series and parallel connection laws.

Results

Series connection		Parallel connection	
V (V)	I (A)	V (V)	I (A)

$R_s =$ $R_p =$
Compare the measured R_1 and R_2 of experiment 1 with that obtained from R_s and R_p of experiment 2.